LAB REPORT

Electronics Lab II (ELC 3910)

Experiment No.: 1

S. No: 1 2

F. No: 2 0 E L B 0 8 4

Name: Y U S U F A H M E D K H A N

Object:

- (a) Positive Clipper
- (b) Combinational Clipper
- (c) Positive Clamper
- (d) Diode Characteristics

Also: Rectifier

Software used: PSpice

Date of performing the experiment: 07/09/2022


Date of report submission: 14/09/2022


Snippets of

I. Code for part (a) [Positive Clipper]

```
*Yusuf
         Ahmed Khan_PART A
   1 0 SIN(0 5V 1\overline{K}HZ)
V1
   \bar{1}
        1K
R1
   2
      3 D1N914
\mathrm{D}\mathrm{A}
   3 0 27
VR
MODEL D1N914 D()
TRAN OMS 40MS
. PROBE
END
```

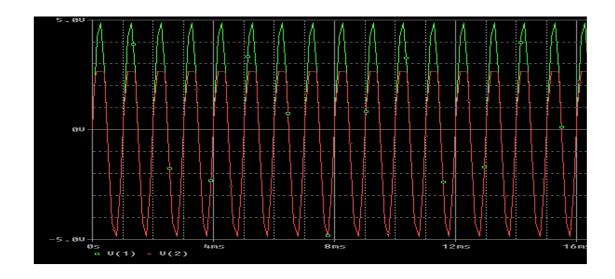II. Plot for part (a) [Positive Clipper] (Input & Output response)



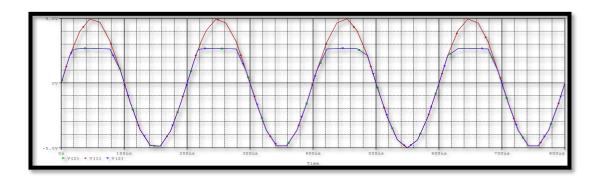



Snippets of

I. Code for part (b) [Combinational Clipper]


```
*Yusuf Ahmed Khan_PART B
V1 1 0 SIN(0 10V 1KHZ)
R1 1 2 1K
DA 2 3 D1N914
DB 4 2 D1N914
VR 3 0 5V
VP 0 4 5V
.MODEL D1N914 D()
.TRAN OMS 40MS
.PROBE
.END
```

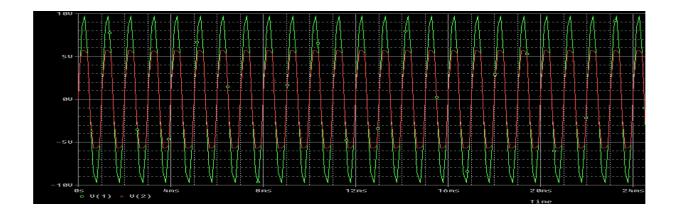II. Plot for part (b) [Combinational Clipper] (Input & Output response)



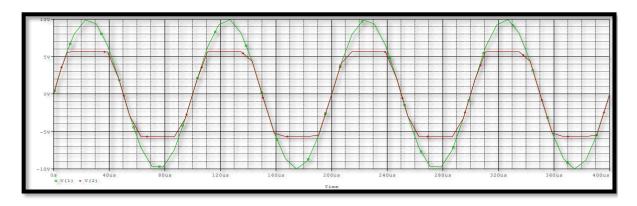

Transfer Characteristics

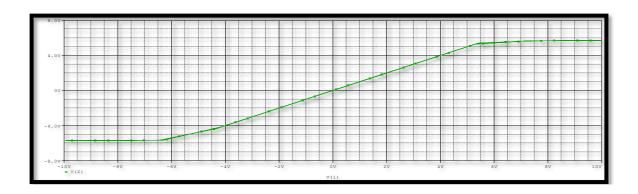


Snippets of

I. Code for part (c) [Positive Clamper]

```
*Yusuf Ahmed Khan_PART C
V1 1 0 SIN(0 5V 1KHZ)
C1 1 2 10UF
R1 2 0 1K
DA 0 2 D1N914
.MODEL D1N914 D()
.TRAN OMS 40MS
.PROBE
.END |
```

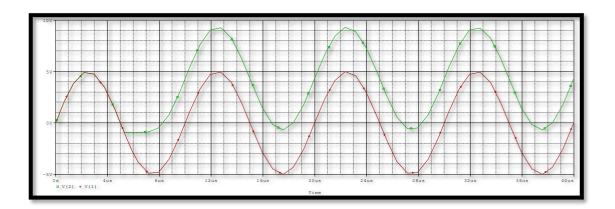II. Plot for part (c) [Positive Clamper] (Input & Output response)




Snippets of

I. Code for part (d) [Diode Characteristics]


```
*Yusuf_Ahmed_Khan_part(d)_DIODE
V 1 0 0V
R1 1 2 1K
D1 2 0 D1N914
.MODEL D1N914 D()
.DC V 0V 75V 5V
.probe
.end
```

II. Plot for part (d) [Diode Characteristics] [I-V Characteristics]

Forward Bias

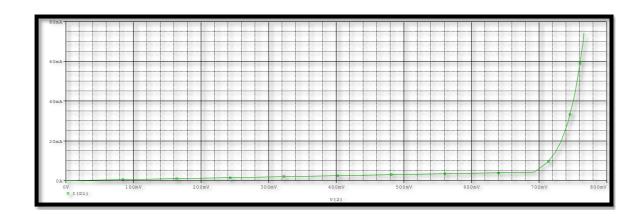

Reverse Bias

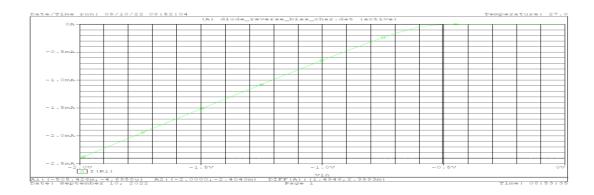

Additional (for practice) >> Rectifier

Code:

```
*Yusuf Ahmed Khan RECTIFIEM
V1 1 0 SIN(0 5V 500HZ)
R1 1 2 1K
DA 2 0 D1N914
.MODEL D1N914 D()
.TRAN 0.1MS 40MS
.PROBE
.END
```

Plot (Input & Output response)

