

# LAB REPORT

## Electronics Lab III (ELC 3910)

Experiment No.: 7

S. No:

1	2
---	---

F. No:

2	0	E	L	B	0	8	4
---	---	---	---	---	---	---	---

Name:

Y	U	S	U	F		A	H	M	E	D		K	H	A	N
---	---	---	---	---	--	---	---	---	---	---	--	---	---	---	---

**Object:**

**Analysis and Simulation of differential amplifier with passive load. Plot the DC transfer characteristics, transient and frequency response. Measure bandwidth input and output resistance.**

**Software used: PSpice**

**Date of performing the experiment: 16/11/2022**

**Date of report submission: 23/11/2022**

## Experiment 7

Part 1, calculate gain

Yusuf Ahmed Khan

```

* Yusuf Ahmed Khan
* Differential amplifier, part 1, calculate gain
VDD 6 0 3.5V
Vin_p 2 0 SIN(777M 1MV 1K)
Vin_n 4 0 SIN(777M -1MV 1K)
R1 6 1 4.375K
R2 6 5 4.375K
IREF 3 0 0.8MA

M1 1 2 3 0 MN W=50U L=0.7U
M2 5 4 3 0 MN W=50U L=0.7U

MODEL MN NMOS (
+TOX = 7.9E-9          NSUB = 1E17          LEVEL = 3
+PHI = 0.7             VTO = 0.5445549       GAMMA = 0.5827871
+UO = 436.256147       ETA = 0                DELTA = 0
+KP = 2.055786E-4      VMAX = 8.309444E4      THETA = 0.1749684
+RSH = 0.0559398       NFS = 1E12            KAPPA = 0.2574081
+KJ = 3E-7             LD = 3.162278E-11      TPG = 1
+CGDO = 2.82E-10       CGSO = 2.82E-10       WD = 7.046724E-8
+CJ = 1E-3             PB = 0.9758533        CGBO = 1E-10
+CJSW = 3.777852E-10   MJSW = 0.3508721      MJ = 0.3448504
)

TRAN 0.1U 3M
TF V(1,5) Vin_n
OP
PROBE
END

```

\*\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

V(1,5)/Vin\_n = 1.029E+01

INPUT RESISTANCE AT Vin\_n = 1.000E+20


OUTPUT RESISTANCE AT V(1,5) = 8.450E+03

JOB CONCLUDED

\*\*\*\*\* 11/16/22 16:00:09 \*\*\*\*\* PSpice 17.2.0 (March 2016) \*\*\*\*\* ID# 0 \*\*\*\*\*

\* Yusuf Ahmed Khan

\*\*\*\*\* JOB STATISTICS SUMMARY

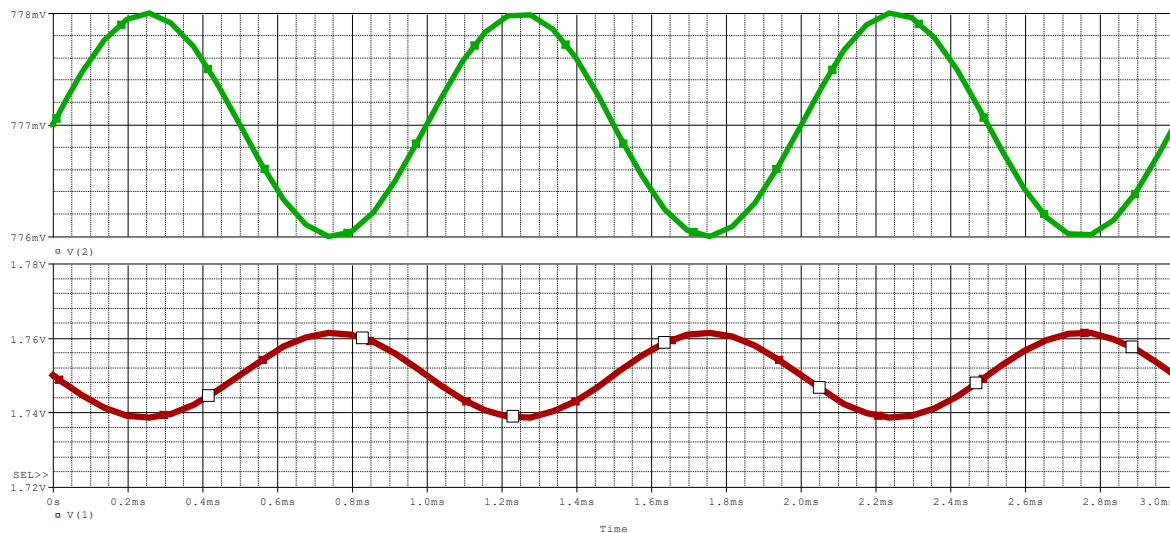

**Part 2, frequency response**

```

* Yusuf Ahmed Khan
* Differential amplifier, part 2, freq response


VDD 6 0 3.5V
Vin_p 2 0 AC 1V
Vin_n 4 0 AC 1V
R1 6 1 4.375K
R2 6 5 4.375K
IREF 3 0 0.8mA

M1 1 2 3 0 MN W=50U L=0.7U
M2 5 4 3 0 MN W=50U L=0.7U

.MODEL MN NMOS (
+TOX      = 7.9E-9          NSUB      = 1E17          LEVEL      = 3
+PHI      = 0.7            VTO       = 0.5445549      GAMMA      = 0.5827871
+UO       = 436.256147     ETA       = 0              DELTA      = 0
+KP       = 2.055786E-4    VMAX     = 8.309444E4      THETA      = 0.1749684
+RSH      = 0.0559398     NFS      = 1E12          KAPPA      = 0.2574081
+XJ       = 3E-7          LD        = 3.162278E-11      TPG        = 1
+CGDO     = 2.82E-10      CGSO     = 2.82E-10      WD         = 7.046724E-8
+CJ       = 1E-3          PB        = 0.9758533      CGBO       = 1E-10
+CJSW     = 3.777852E-10 MJSW     = 0.3508721      MJ         = 0.3448504
)

*.TRAN 0.1U 3M
.TF V(1,5) Vin_n
.AC DEC 100 1HZ 100MEGHZ
.OP
.PROBE
.END

```

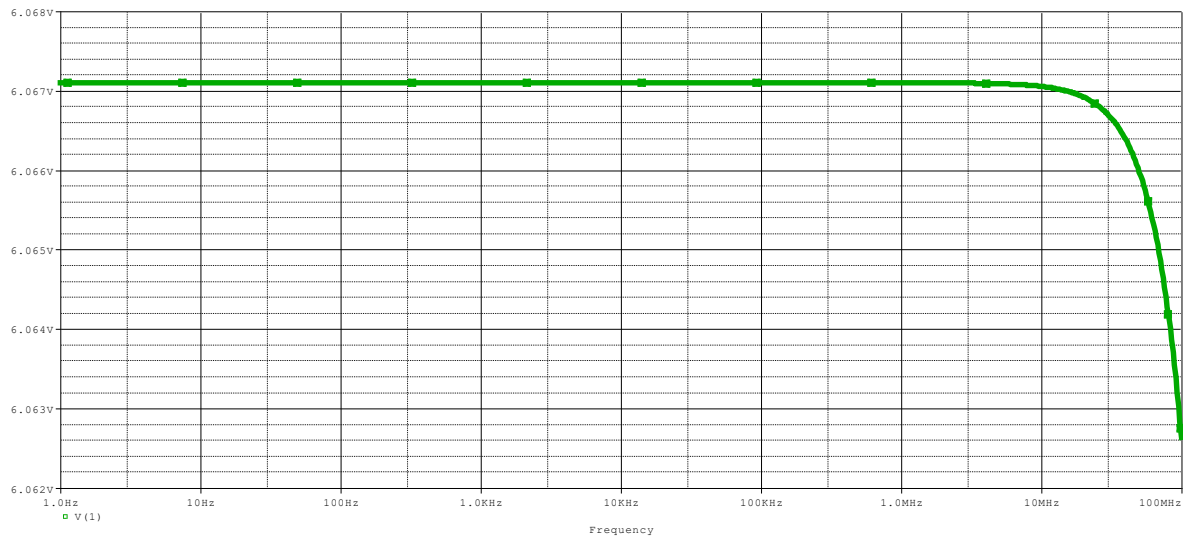

### Part 3 bandwidth calculation

```

VDD 6 0 3.5V
Vin_p 2 0 AC 1V
Vin_n 4 0 AC -1V
R1 6 1 4.375K
R2 6 5 4.375K
IREF 3 0 0.8mA

M1 1 2 3 0 MN W=50U L=0.7U
M2 5 4 3 0 MN W=50U L=0.7U

.MODEL MN NMOS (
+TOX      = 7.9E-9          NSUB      = 1E17          GAMMA    = 0.5827871
+PHI      = 0.7            VTO       = 0.5445549      DELTA    = 0
+UO       = 436.256147     ETA       = 0.5445549      THETA    = 0.1749684
+KP       = 2.055786E-4     VMAX    = 8.309444E4      KAPPA    = 0.2574081
+RSH      = 0.0559398      NFS     = 1E12          TPG      = 1
+XJ       = 3E-7           LD        = 3.162278E-11     WD       = 7.046724E-8
+CGDO     = 3.82E-10       CGSO    = 2.82E-10       CGBO     = 1E-10
+CJ       = 1E-3           PB        = 0.9758533      MJ       = 0.3448504
+CJSW     = 3.777852E-10  MJSW    = 0.3508721      )

*.TRAN 0.1U 3M
.TF V(1.5) Vin_n
.AC DEC 100 1HZ 1000000MEGHZ
.OP
.PROBE
.END

```

